

22. If the total power dissipated in the circuit shown in the Fig. 1.113 is 18 watts, find the value of R and current through it.

(Ans. : $12\Omega, 0.6\text{ A}$)

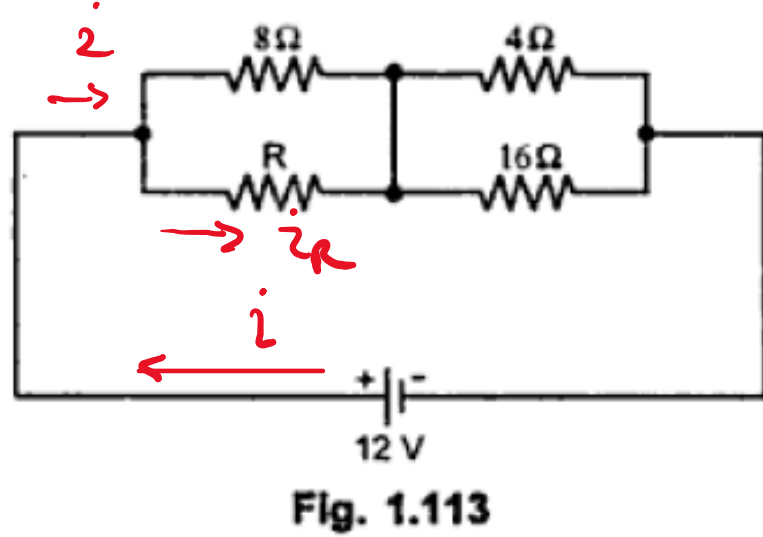


Fig. 1.113

The total power dissipated in the circuit is equal to the power generated by the power source

$$P_{\text{anti}} = P_{\text{source}} = Vi = 12 \times i = 18 \text{ Watts} \Rightarrow$$



$$12i = 18 \Rightarrow i = \frac{18}{12} = \frac{6 \times 3}{6 \times 2} = \frac{3}{2} \text{ A}$$

Next, you need to find the equivalent resistance

Remember The equivalent resistance of two parallel resistance



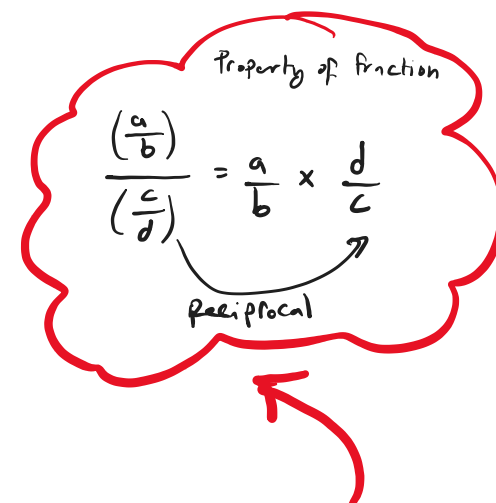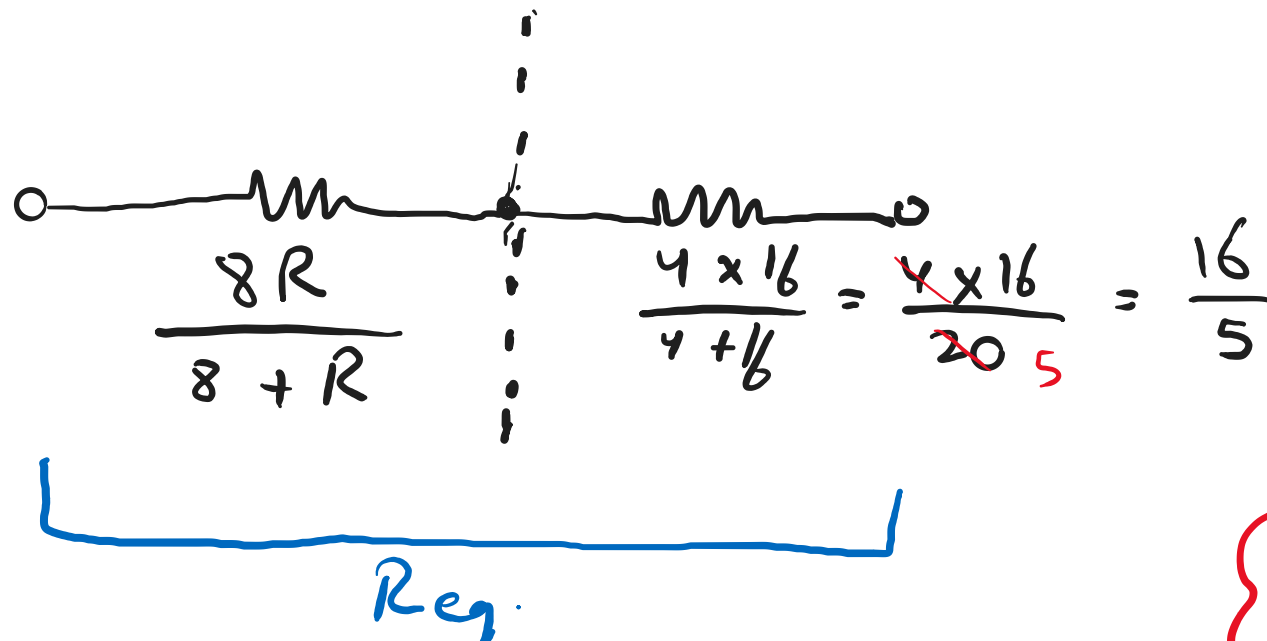The equivalent resistance in the above figure is



$$R_{eq} = \frac{8R}{8+R} + \frac{16}{5}$$

Also note that $R_{eq} = \frac{V_s}{i} = \frac{12}{3/2} = 12 \times \frac{2}{3} = 8\Omega$

$$8 = \frac{8R}{8+R} + \frac{16}{5} = 8 \left[\frac{R}{8+R} + \frac{2}{5} \right]$$

$$1 = \frac{R}{8+R} + \frac{2}{5} \Rightarrow \frac{R}{8+R} = 1 - \frac{2}{5}$$


$$\frac{R}{R+8} = \frac{3}{5} \Rightarrow 5R = 3(R+8)$$

$$5R = 3R + 24 \Rightarrow 5R - 3R = 24$$

$$2R = 24 \Rightarrow \boxed{R = 12\Omega}$$

To find the current through (R) we need to calculate the voltage drop across R , which is the same voltage drop across the first parallel pair of resistors, i.e.,

The equivalent circuit can be drawn as

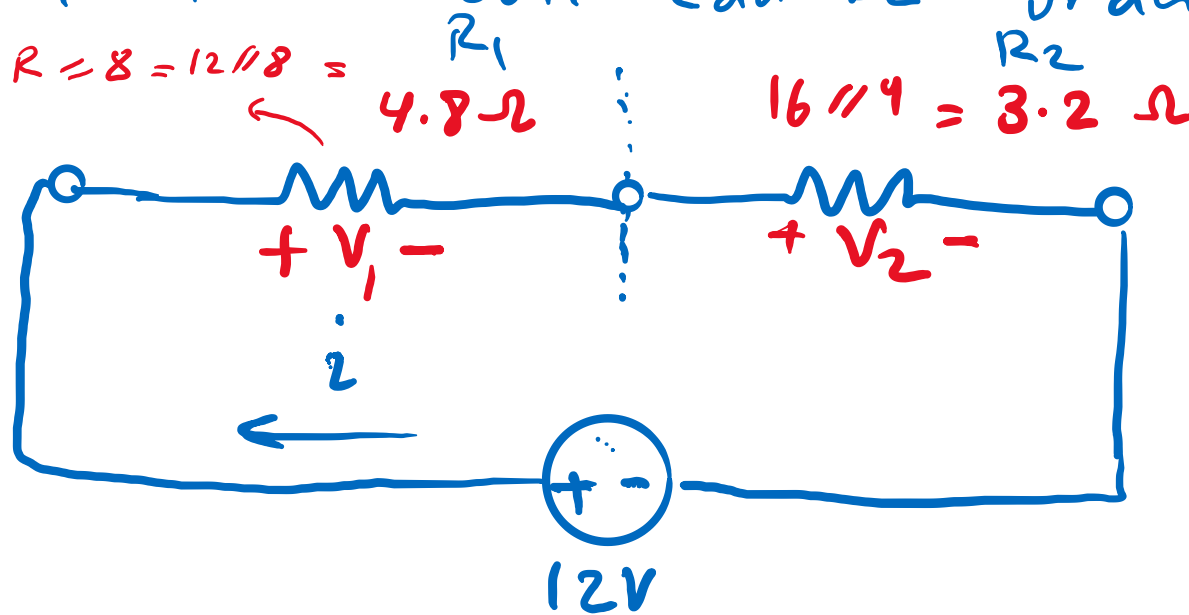

Using the voltage divider rule:

$$V_1 = V_s \frac{R_1}{R_1 + R_2} = 12 \times \frac{4.8}{4.8 + 3.2} = 12 \times \frac{4.8}{8} = 7.2 \text{ V}$$

which is the same voltage across R

$$i_R = \frac{V_R}{R} = \frac{7.2}{12} = \boxed{0.6 \text{ A}}$$